

## 5.7 Sequential Assignment Statements

- There are two styles of hardware modelling: structural and behavioral.
- Behavioral is further divided into data flow (use nonprocedural concurrent statements) and algorithmic (use procedural sequential statements) descriptions.

### 5.7.1 process Statement


- The **process** statement is used to separate sequential statements in VHDL from concurrent statements.
- It encloses a section of sequential statements that exists inside an architecture.
- The sequential statements are executed in a procedural fashion from top to bottom.
- It is possible to have more than one process in an architecture, in which case the processes interact concurrently.
- The statements in a process execute in an infinite loop which may be pause with a **wait** statement. The process therefore has an implicit infinite **do-loop**.

- The syntax of a process is:

```
[PROCESS_LABEL:]  
process [(SIGNAL_NAME {, SIGNAL_NAME})] -- Sensitivity list  
  -- Declarative part (only available within the process)  
  [variable declarations]  
begin  
  -- Statement part  
  [Simple signal assignment statements]  
  [Variable assignment statements]  
  [if statements]  
  [case statements]  
  [loop statements]  
  [wait statement]  
end process [PROCESS_LABEL];
```

- The two architectures on the following slide perform the same functionality.
- However, HB1 contains a conditional concurrent statement, while in HB2 this statement is defined in a process statement. The process waits for a change in J, K, Q, or Q\_BAR.

## A JK-Latch Example

 

```
entity JK_LATCH is
  port (J, K : in BIT;
        Q : inout := '0';
        Q_BAR : inout := '1');
end JK_LATCH;

architecture BH1 of JK_LATCH is
begin
  Q <= Q when (J='0' and K='0') else
    '0' when (J='0' and K='1') else
    '1' when (J='1' and K='0') else
    Q_BAR;
  Q_BAR <= not Q;
end BH1;
```

```
architecture BH2 of JK_LATCH is
begin
  process
  begin
    if (J='0' and K='0') then
      Q <= Q;
    elsif (J='0' and K='1') then
      Q <= '0';
    elsif (J='1' and K='0') then
      Q <= '1';
    else
      Q <= Q_BAR;
    end if;

    wait on J, K, Q, Q_BAR;
  end process;
  Q_BAR <= not Q;
end BH2;
```

## if, case and loop Statements

- These are sequential statements used for purposes of selection and repetition in the programming code.
- For the **if** statement, the condition expressions are evaluated in order until one is met. For the **case** statement, all alternatives have equal priority.
- Syntax of **if**:

```
if expression then
    statement;
    { statement; }
elseif expression then
    statement;
    { statement; }
else
    statement;
    { statement; }
end if;
```

- Syntax of **case**:

```
case expression is
    when constant_value =>
        statement;
        { statement; }
    when constant_value =>
        statement;
        { statement; }
    when others =>
        statement;
        { statement; }
end case;
```

- There are three forms of the **loop** statement in VHDL. Each have the following syntax:
- The **for-loop** executes a set of sequential statements a certain number of times:

```
[LOOP_LABEL:]  
for variable_name in range loop  
    statement;  
    { statement; }  
end loop [LOOP_LABEL];
```

- The **while-loop** repeatedly executes a set of statements while the condition is satisfied:

```
[LOOP_LABEL:]  
while boolean_expression loop  
    statement;  
    { statement; }  
end loop [LOOP_LABEL];
```

- The infinite-loop is similar to the above, but simply uses the **loop** statement alone. i.e.:

```
[LOOP_LABEL:]  
loop  
    statement;.....
```

## The Use of Variables in a process

- **variable** data objects are not related to a wire in a circuit.
- Variables can be use in ways that **signal** objects can't.
- Values are assigned to variables using the `:=` operator, rather than the `<=` operator used for signals.
- For example, let us consider a design which counts the number of 1's in a 3-bit input:

---

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity NUMBITS is
  port(X : in STD_LOGIC_VECTOR(1 to 3);
        Count : buffer INTEGER range 0 to 3);
end NUMBITS;
```

---

```
architecture BEHAVIOUR of NUMBITS is
begin
  process (X)      -- count the number of bits in X with the value 1
  begin
    Count <= 0;    -- the 0 with no quotes is a decimal number
    for I in 1 to 3 loop
      if X(I) = '1' then
        Count <= Count+1;
      end if;
    end loop;
  end process;
end BEHAVIOUR;
```

---

- Here, the signal Count is defined as **buffer** because it is used on the right hand side of the equation.
- This does not represent a sensible circuit with the "Count <= Count+1" type of statement since Count will be an unstable signal. The code should be modified as follows.

```
library ieee;
use ieee.std_logic_1164.all;

entity NUMBITS is
    port(X : in STD_LOGIC_VECTOR(1 to 3); Count : out INTEGER range 0 to 3);
end NUMBITS;

architecture BEHAVIOUR of NUMBITS is
begin
    process (X)    --count the number of bits in X with the value 1
        variable Tmp : INTEGER;
    begin
        Tmp := 0;    -- The assignment of variable is :=
        for I in 1 to 3 loop
            if X(I) = '1' then
                Tmp := Tmp + 1;
            end if;
        end loop;
        Count <= Tmp;
    end process;
end BEHAVIOUR;
```


```
library ieee;
use ieee.std_logic_1164.all;

entity NUMBITS is
  port(X : in STD_LOGIC_VECTOR(1 to 3); Count : out INTEGER range 0 to 3);
end NUMBITS;

architecture BEHAVIOUR of NUMBITS is
begin
  process (X)    --count the number of bits in X with the value 1
    variable Tmp : INTEGER;
  begin
    Tmp := 0;    -- The assignment of variable is :=
    for I in 1 to 3 loop
      if X(I) = '1' then
        Tmp := Tmp + 1;
      end if;
    end loop;
    Count <= Tmp;
  end process;
end BEHAVIOUR;
```



 - We may implement this design with a hardware circuit. For example, a full adder:



### 5.7.4 The wait Statement and Sensitivity List

- Execution of sequential statements in a process can be paused with a **wait** statement.
  - **wait on** X; – Wait for the signal X to change value.
  - **wait until** (X = '1'); – Wait until the signal X changes to the value 1.
  - **wait for** 4 ms; – Wait for a period of time (4 ms) before continuing.
- Alternatively, a sensitivity list follows the **process** statement. Both of the following function the same by waiting for a change in ALARM\_A or ALARM\_B:

<pre> process (ALARM_A, ALARM_B) begin     ... end           </pre>	<pre> process begin     ...     wait on ALARM_A, ALARM_B; end           </pre>
---	--

- When using a sensitivity list, we may not use any **wait** statements in the process.

## 5.8 Register and Simple Sequential Circuit Descriptions

### 5.8.1 D Latch and D Flip-Flop

- Latches trigger on a clock level, while flip-flops trigger on a clock edge.

```
library ieee;                                -- D latch definition.
use ieee.std_logic_1164.all;
entity latch is
  port(D, clk : in STD_LOGIC; Q : out STD_LOGIC);
end latch;
```

```
architecture Behaviour of latch is
begin
  process (D, clk)
  begin
    if clk = '1' then
      Q <= D;
    end if
  end process;
end Behaviour;
```

- D flip-flop definition:

```
library ieee;                                -- D flip-flop definition.
use ieee.std_logic_1164.all;

entity flipflop is
    port(D, clk : in  STD_LOGIC;
         Q      : out STD_LOGIC);
end flipflop;


architecture Behaviour of flipflop is
begin
    process (clk)
    begin
        if clk'EVENT and clk = '1' then
            Q <= D;
        end if
    end process;
end Behaviour;
```

### 5.8.3 An Example 4-bit Register

```
library ieee;                                -- A four-bit register.
use ieee.std_logic_1164.all;

entity reg4 is
  port(D : in STD_LOGIC_VECTOR(3 downto 0);
        Resetn, clk : in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR(3 downto 0));
end reg4;

 architecture Behaviour of reg4 is
begin
  process (Resetn, clk)
  begin
    if Resetn = '0' then
      Q <= "0000";          -- or Q <= (others => '0');
    elsif clk'EVENT and clk = '1' then
      Q <= D;
    end if;
  end process;
end Behaviour;
```




- Question: How to modify the above code so it represents an n-bit register?

## 5.8.4 An Example Shift Register

```
library ieee;                                -- A four-bit shift register.
use ieee.std_logic_1164.all;

entity shift4 is
  port(w, clk : in  STD_LOGIC;
        Q      : out STD_LOGIC_VECTOR(1 to 4));
end shift4;

 architecture Behaviour of shift4 is
  signal Sreg : STD_LOGIC_VECTOR(1 to 4);
begin
  process (clk)
  begin
    if clk'EVENT and clk='1' then
      Sreg(1) <= Sreg(2);
      Sreg(2) <= Sreg(3);
      Sreg(3) <= Sreg(4);
      Sreg(4) <= w;
    end if;
  end process;
  Q <= Sreg;
end Behaviour;
```



## 5.8.5 An Example 4-bit Counter

```
library ieee;                                -- A four-bit counter.
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity count4 is
  port(Resetn, E, clk : in  STD_LOGIC;
       Q : out STD_LOGIC_VECTOR (3 downto 0));
end count4;

architecture Behaviour of count4 is
  signal Count : STD_LOGIC_VECTOR (3 downto 0);
begin
  process (clk, Resetn)
  begin
    if Resetn = '0' then
      Count <= "0000";
    elsif (clk'EVENT and clk = '1') then
      if E = '1' then
        Count <= Count + 1;
      end if;
    end if;
  end process;
  Q <= Count;
end Behaviour;
```

